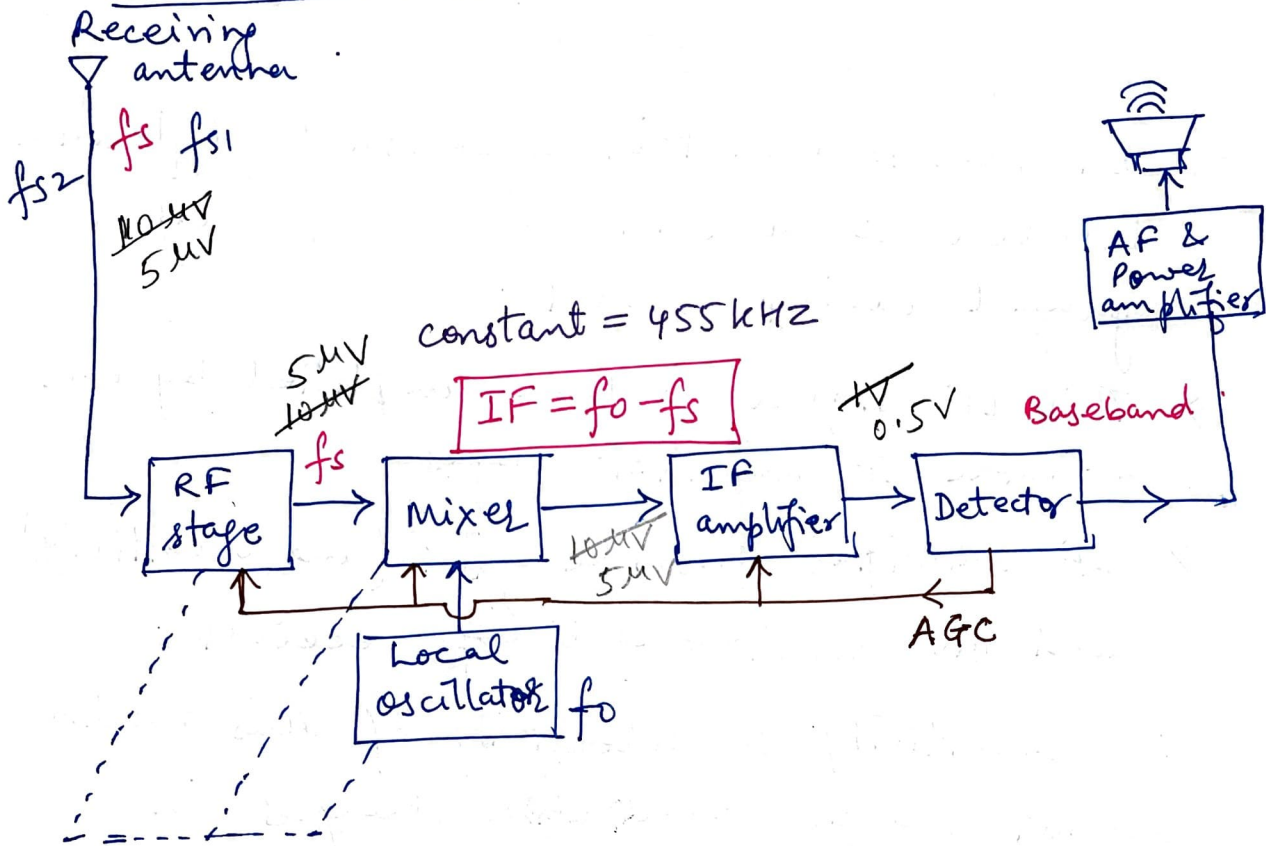


SUPERHETERODYNE RECEIVERS

- Problems in TRF-Rx solved by converting every selected RF signal to a fixed lower frequency signal called Intermediate Frequency (IF)
- This frequency contains same amount of modulation.
- IF signal is then amplified and demodulated to get back the modulating signal.
- As $IF < \text{lowest RF frequency}$, possibility of oscillations and instability is minimized.
- Also, the required value of Q for constant BW does not depend on frequency of desired signal because IF is constant and it is same for all incoming RF signal.
 - ⇒ Selectivity is not hampered.
- ∴ SH-Rx solves all problems associated with TRF-Rx.

BLOCK DIAGRAM OF SH-Rx



Tuned Tuning

- RF stage is used to select wanted/desired signal, reject all other signals and hence reduce the effect of noise.
- We get a signal of frequency, f_s at output of RF amplifier.
- Mixer receives signal from RF stage (f_s) and local oscillator (f_o)
- These two signals are mixed together to produce IF,
ie. $IF = (f_o - f_s)$


Typically, $IF = 438 - 465 \text{ KHz}$

$IF = 455 \text{ KHz}$

- In order to maintain a constant difference between LO and incoming frequency, ganged tuning is used.
- This IF signal is then amplified by one or more IF amplifier stages.
- IF amplifier provide gain (and sensitivity) and BW requirement of receiver.
- ∴ Sensitivity & Selectivity of this receiver do not change much with changes in incoming frequency.
- Amplified IF signal is detected by the detector to recover original modulating signal.
- This is then amplified using audio and power amplifiers & given to loudspeakers.
- AGC → Automatic Gain Control.
This circuit controls the gain of RF & IF stages to maintain constant output.

— IMAGE FREQUENCY REJECTION —

→ SH-Rx — Superheterodyne Receiver.

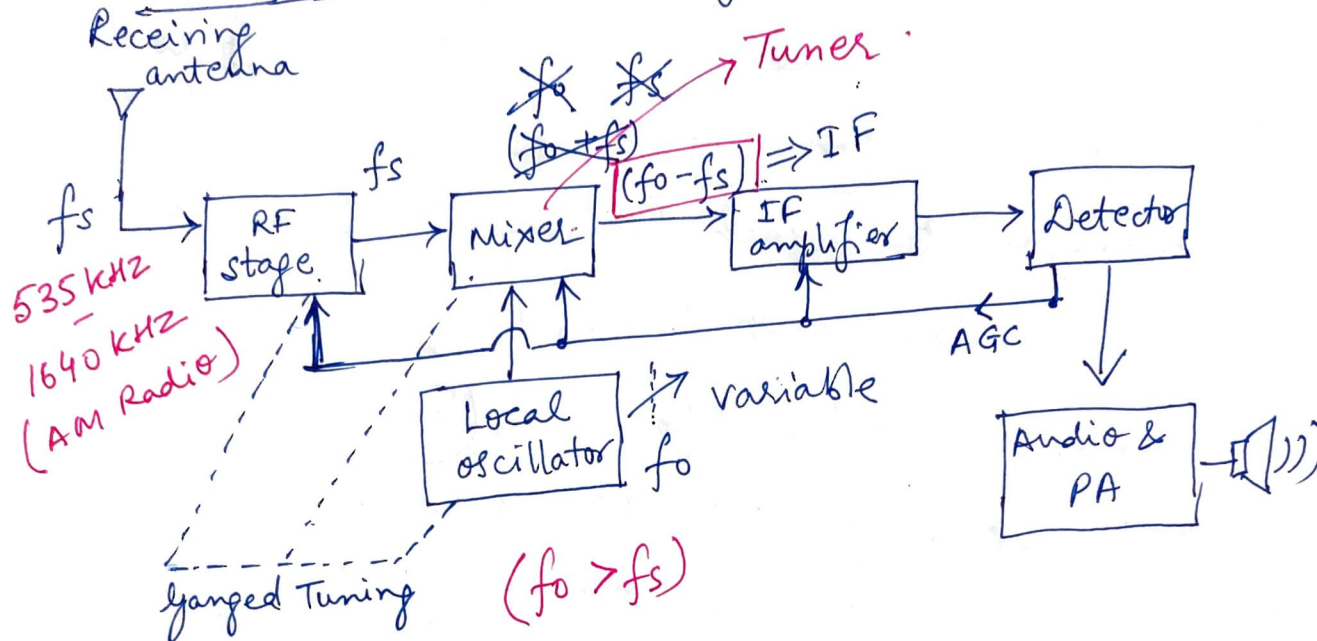

→ IF → 455 KHz

$$f_s \rightarrow 535 \text{ KHz} \Rightarrow f_o = 990 \text{ KHz}$$

$$f_s \rightarrow 1640 \text{ KHz} \Rightarrow f_o = 2095 \text{ KHz}$$

→ In broadcast AM-Rx,

$$f_o > f_s \text{ by IF}$$

$f_o \rightarrow$ local oscillator frequency
 $f_s \rightarrow$ incoming signal frequency

$$\Rightarrow f_o = f_s + \text{IF}$$

$$\Rightarrow \boxed{\text{IF} = (f_o - f_s)}$$

→ Output of mixer → $f_o, f_s, (f_o + f_s), (f_o - f_s)$
 Out of these, $(f_o - f_s)$ is only selected using a tuned circuit after the mixer.

→ Image frequency and its Rejection -

→ Let us assume LO frequency is set to f_0 and unwanted signal, $f_{si} = (f_0 + IF)$ manages to reach the input of mixer.

→ Then, mixer output will be -

$$f_0, (f_0 + IF), 2f_0 + IF, IF$$

This last component, IF is actually the difference between f_{si} & f_0 .

This component will also be amplified by IF amplifier along with the desired signal, at frequency, f_s .

→ This will create interference because both the station corresponding to frequency f_s and f_{si} will be tuned at the same position.

→ This unwanted signal at frequency, f_{si} is known as image frequency and it is said to be the image of signal frequency, f_s .

→ Relation between f_s and f_{si} —

$$IF = (f_o - f_s)$$

$$\Rightarrow f_o = (f_s + IF) \text{ ————— (1)}$$

We also know,

$$f_{si} = (f_o + IF)$$

From (1),

$$f_{si} = ((f_s + IF) + IF)$$

$$f_{si} = f_s + 2IF$$

→ Remedy —

→ Image frequency must be rejected by the receiver.

→ Image rejection depends on front end selectivity of receiver, i.e. selectivity of the RF circuit.

→ Also, image rejection must be achieved before IF stage because once it reaches IF stage, it cannot be removed.

→ Use of RF amplifier improves image frequency rejection.

→ Double Spotting -

→ Let us understand this with an example -

→ Assume, We select IF of SH-Rx to be 470 kHz.

→ Assume a strong station at $f_s = 1640$ kHz

(a) Corresponding, $f_o = 2110$ kHz

$$(\because 2110 - 1640 = 470) = \text{IF.}$$

Hence, strong station will be picked up.


(b) I want to tune to 700 kHz.

then, $f_o = 1170$ kHz ($\because 1170 - 700 = 470$) = IF

(IDEAL) → expected to pick 700 kHz

But...

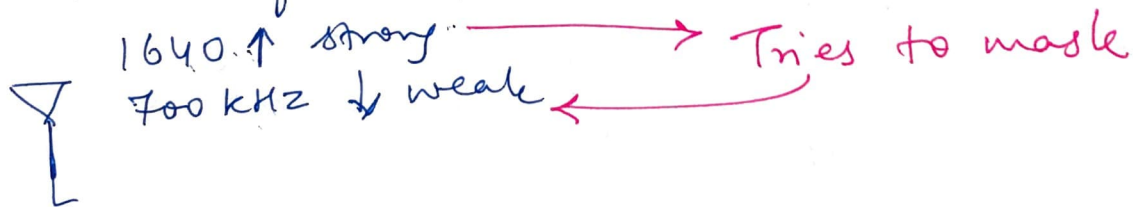This signal, $f_s = 700$ kHz is very weak



$$f_o = 1170$$

→ Now, when 1170 kHz of LO frequency is present, 1640 kHz signal will also beat with this f_o .

$$(1640 - 1170) = 470 \text{ kHz}$$

Hence, this station will also get picked up at this point on the dial.

→ Image rejection using a single tuned circuit-

→ Rejection of image frequency by a single tuned circuit is given by -

$$\alpha = \frac{\text{gain at signal frequency}}{\text{gain at image frequency}}$$

$$\alpha = \sqrt{1 + Q^2 \delta^2}$$

where, $Q \rightarrow$ loaded Q of tuned circuit

$$\delta = \left[\frac{f_{si}}{f_s} - \frac{f_s}{f_{si}} \right]$$


→ If the receiver has an RF stage, then there will be two tuned circuits both of them tuned to f_s .

→ Rejection can then be calculated using same formula and total rejection will be the product of individual rejection introduced by individual tuned circuits.

Q1. In a SH-Rx having no RF amplifier, the loaded Q of antenna coupling circuit (at the input of mixer) is 90. If IF is 455 kHz, calculate -

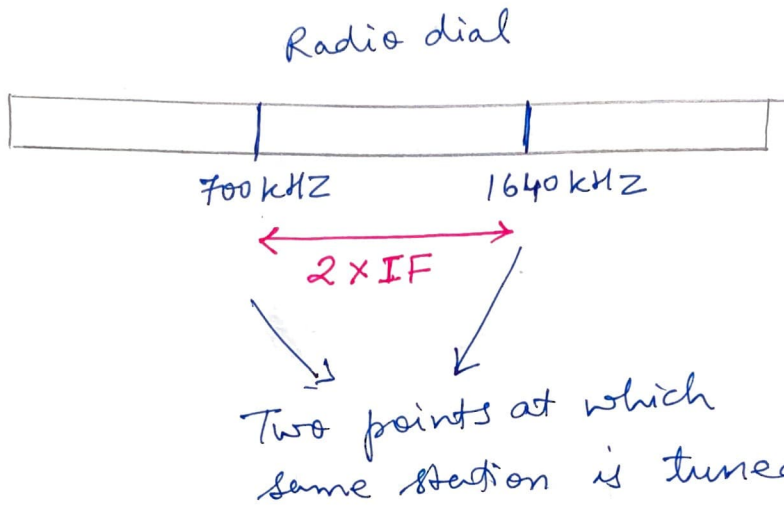(a) Image frequency and image frequency rejection ratio at 950 kHz

→ 700 kHz is weak and hence is masked by a strong signal at 1640 kHz



- Double spotting means the same station gets picked up at two different nearby points on the receiver dial.
- It is due to poor front end selectivity i.e. inadequate image frequency rejection.
- It is harmful because a weak station may be masked by reception of a strong station at the same point, on the dial.
- It can be reduced by increasing front end selectivity of receiver.
- Inclusion of RF amplifier stage will help in avoiding double spotting.

b) Image frequency and its rejection at 10 MHz.

Soln. (a) $Q = 90$ $IF = 455 \text{ kHz}$ $f_s = 950 \text{ kHz}$

$$\begin{aligned} f_{si} &= f_s + 2IF \\ &= 950 + (2 \times 455) \\ &= 1860 \text{ kHz} \end{aligned}$$

$$\Rightarrow \alpha = \sqrt{1 + Q^2 \beta^2} = \sqrt{1 + (90^2 \times 1.45^2)} = \boxed{130.5} \text{ good rejection}$$

$$\left[\begin{array}{l} \text{We know,} \\ \beta = \frac{f_{si}}{f_s} - \frac{f_s}{f_{si}} = \frac{1860}{950} - \frac{950}{1860} = 1.45 \end{array} \right]$$

(b) $Q = 90$ $IF = 455 \text{ kHz}$ $f_s = 10 \text{ MHz}$

$$\begin{aligned} f_{si} &= f_s + 2IF = 10 + (2 \times 0.455) \\ &= 10.91 \text{ MHz} \end{aligned}$$

$$\beta = \frac{f_{si}}{f_s} - \frac{f_s}{f_{si}} = \frac{10.91}{10} - \frac{10}{10.91} = 0.174$$


$$\Rightarrow \alpha = \sqrt{1 + Q^2 \beta^2} = \sqrt{1 + (90^2 \times 0.174^2)} = \boxed{15.72} \text{ pretty less rejection.}$$

→ Without RF amplifier, image rejection is adequate at low frequency. However, it is inadequate at higher frequency.
∴ RF amplifier may be used at high freq.

Q2: In order to make image frequency rejection of receiver of previous example as good as 950 kHz for 10 MHz as well, calculate the loaded Q which an RF amplifier for this receiver would have to use.

$$f_s = \underline{10 \text{ MHz}}$$

Soln:

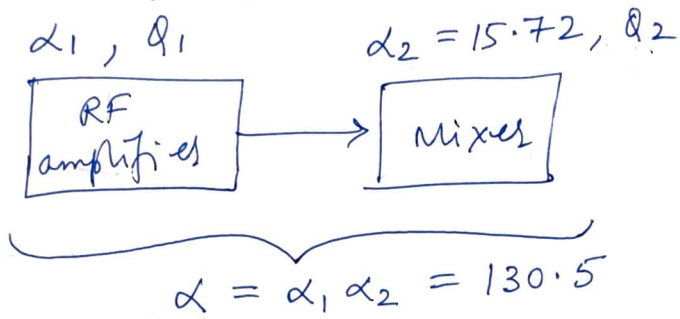

$$\alpha_1 = \frac{\alpha}{\alpha_2} = \frac{130.5}{15.72} = 8.3$$

$$\alpha_1 = \sqrt{1 + Q_1^2 S_1^2}$$

Substituting, $S = 0.174$

$$\Rightarrow Q = 47.35 \rightarrow \text{value of loaded } Q \text{ of RF amplifier.}$$

→ A well designed receiver would have same Q for tuned circuits of mixer and RF amplifier.

$$\therefore Q_1 = Q_2 = \text{geometric mean of } 90 \text{ and } 47.35$$

$$= \sqrt{90 \times 47.35} = 65.28$$

3. With respect to previous example, calculate the new IF that would be needed if RF amplifier is not to be used.

Soln. At 950 kHz, $\beta = 1.45$ $\alpha = 130.5$

~~Let new f_{si}~~

Let new value of image frequency be f_{si}'

We know,

$$\beta = \frac{f_{si}}{f_s} - \frac{f_s}{f_{si}}$$

$$\Rightarrow 1.45 = \frac{1860}{950} - \frac{950}{1860} = \frac{f_{si}'}{10 \text{ MHz}} - \frac{10 \text{ MHz}}{f_{si}'}$$

By equating,

$$\frac{f_{si}'}{10 \text{ MHz}} = \frac{1860}{950} = 1.9578$$

$$\Rightarrow f_{si}' = f_s + 2 \text{ IF}'$$

$$\Rightarrow \text{IF}' = \frac{19.578 - 10}{2} = 4.789 \text{ MHz}$$

\Rightarrow Increase in image frequency will improve image rejection.